

USN

--	--	--	--	--	--	--	--	--	--

**RV COLLEGE OF ENGINEERING®**

(An Autonomous Institution Affiliated to VTU)

I Semester B. E. Regular / Supplementary Examinations Feb/Mar-2025

**PRINCIPLES OF ELECTRONICS ENGINEERING**

Time: 03 Hours

Maximum Marks: 100

Instructions to candidates:


1. Answer all questions from Part A. Part A questions should be answered in first three pages of the answer book only.
2. Answer FIVE full questions from Part B. In Part B question number 2 is compulsory. Answer any one full question from 3 and 4, 5 and 6, 7 and 8 & 9 and 10.

**PART-A****M BT CO**

1	1.1	In a regulated DC power supply the output voltage drops from 12V to 11.8V when the input voltage reduces by 10%. The line regulation is _____.	01	1	1
	1.2	The input to a full wave bridge rectifier with a filter of $100\mu F$ is $100 \sin 314t$ and the load resistance of $900\Omega$ . The DC output voltage is _____.	01	1	2
	1.3	An NPN transistor has $I_{CO} = 25nA$ , $I_B = 0$ , $V_{CE} = 4V$ and $I_C = 20\mu A$ . The value of $\beta$ is _____.	01	2	2
	1.4	Three amplifiers with voltage gain of 20, 100 and 2000 are connected in cascade, the overall gain in dB = _____.	01	1	2
	1.5	The Slew rate of an Op - Amp is $3V/\mu sec$ with a peak value of voltage as 2V. Calculate the maximum output frequency so that the output is not distorted.	01	1	2
	1.6	In a RC phase shift oscillator circuit using an ideal voltage amplifier with $C = 0.01\mu F$ and $R = 2K\Omega$ . The frequency of oscillation is _____ KHz.	01	2	2
	1.7	An op-Amp has a differential gain of 86dB and Common mode gain of 20dB. The CMRR in dB is _____.	01	1	1
	1.8	A non-inverting amplifier using an op-amp has $R_i = 10K\Omega$ and $R_f = 40K\Omega$ . The closed loop gain is _____.	01	1	1
	1.9	In a 3 variable K - map, if all the cells contain 1's then the output is _____.	01	1	1
	1.10	The minimized form of logic expression: $A'B'C' + A'BC' + A'BC + ABC'$ is _____.	01	2	2
	1.11	If one of the input to a 2 - input EX - NOR gate is connected to 0, then it can be used as _____.	01	1	1
	1.12	The Hexadecimal equivalent of $(536)_8$ is _____.	01	1	1
	1.13	The total power delivered by an amplitude modulated wave is 2640W. If the modulation index = 0.8, the power in each side bands = _____ W.	01	1	2
	1.14	In a voltage follower circuit, the op-amp is ideal in all respect except that it has a finite gain of 400. The % error in the gain of the voltage follower with respect to its ideal value is equal to _____.	01	2	2
	1.15	An audio signal of 2KHz is used to amplitude modulate the carrier of 600KHz. The bandwidth required is _____ KHz.	01	1	1

1.16	The value of intermediate frequency in super heterodyne receiver is _____ KHz.	01	1	1
1.17	Convert the binary number $(1010101)_2$ to octal.	01	1	1
1.18	The device which converts energy from one form to another form is called _____.	01	1	1
1.19	Differentiate between Sensors and Transducers.	02	1	2

### PART-B

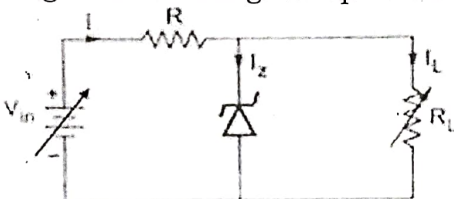2	a	A full wave bridge rectifier drives a load resistance of $150\Omega$ in parallel with a filter capacitor $C$ . If the ac input to the rectifier is $150V$ at $100Hz$ , calculate the capacitor value needed so that the ripple factor is 2%. Determine the output dc voltage, peak to peak ripple voltage and the load regulation.	05	2	2
	b	Briefly explain the three regions of operation of a <i>BJT</i> . Draw and explain the input and output characteristics of a <i>BJT</i> in Common Emitter Configuration.	05	1	1
	c	Design the Zener Regulator for the given specifications:  $V_{in}$ varies from $12V$ to $18V$ $R_L$ varies from $225\Omega$ to $1.8K\Omega$ $V_Z = 9V$ $I_{Z(min)} = 10mA$ $P_{d(max)} = 4.5W$	06	3	4
3	a	Explain the operation of <i>RC</i> phase shift oscillator with a circuit diagram and also calculate the frequency of oscillation if $R = 5K\Omega$ and $C = 0.01\mu F$ .	08	1	1
	b	Draw the circuit and design the values of a summer circuit using 2 ideal op-amps to get an output voltage $V_0 = V_1 - 2V_2 - 4V_3 + 6V_4 + 8V_5$ where $V_1, V_2, V_3, V_4$ and $V_5$ are the available input voltages.	08	3	4
		<b>OR</b>			
4	a	Draw the circuit of an integrator using an op-amp and derive the expression for the output voltage.	08	1	1
	b	An amplifier has a gain of $50dB$ . The bandwidth of $250KHz$ , distortion of $12\%$ , an input impedance of $30K\Omega$ , and an output impedance of $2K\Omega$ . If the voltage series negative feedback of $2.9\%$ is given to this amplifier, calculate the gain, input impedance, output impedance, bandwidth, and distortion of the amplifier with negative feedback.	08	2	3
5	a	Write the truth table for " <i>SUM</i> " and " <i>CARRYOUT</i> " of a full adder. From the truth table, obtain the expressions for the same and realize the full adder using 2 half adders.	08	2	1

6	b	Simplify the logic expression using K map and implement the logic circuit using NAND Gate. $F = \sum m(0,1,2,3,5,7,8,9,10,12,13)$ <b>OR</b>	08	3	3
	a	Simplify the following expression and realize using basic gates i) $Y = (A + B)(A + B)(A + B)$ ii) $Y = XY + XYZ + XY\bar{Z} + \bar{X}YZ$	06	1	2
	b	Subtract the given number using 2's complement method i) $(9)_{10} - (7)_{10}$ ii) $(3)_{10} - (6)_{10}$	04	2	2
	c	Perform the following: i) Convert $(475.25)_8$ to its decimal equivalent ii) Convert $(3509)_{10}$ to its hexadecimal equivalent	06	1	2
7	a	Differentiate between <i>RISC</i> and <i>CISC</i> architecture.	08	1	2
	b	A carrier of 2MHz has 1KW of its power amplitude modulated with a sinusoidal signal of 2KHz. The depth of modulation is 60%. Calculate the sideband frequencies, the signal bandwidth, the power in the sidebands and total power in the modulated wave. <b>OR</b>	08	2	3
8	a	With the help of a block diagram, explain the working of super heterodyne receiver.	08	1	1
	b	Differentiate between Harvard and <i>Von – Neumann CPU</i> architecture.	08	1	1
9	a	Explain the working principle of the following sensors and mention its applications. i) Humidity sensor ii) Ultrasonic sensor.	08	2	1
	b	Biomedical sensors are widely used to monitor various parameters of the human body. Mention any such 4 parameters of human body for which Biomedical sensors can be used, also mention the details of the sensors used for measuring these parameters. <b>OR</b>	08	1	2
	a	Explain the following with examples: i) Active sensor ii) Passive sensor	08	2	1
	b	Describe i) Piezo-electric Transducer ii) Hall Effect transducer.	08	1	1