

**RV COLLEGE OF ENGINEERING®**

(An Autonomous Institution affiliated to VTU)

I / II Semester B. E. Regular / Supplementary Examinations Feb-2024

Common to all programs

**BASICS OF ELECTRICAL ENGINEERING****Time: 03 Hours****Maximum Marks: 100****Instructions to candidates:**

1. Answer all questions from Part A. Part A questions should be answered in first three pages of the answer book only.
2. Answer SIX full questions from Part B. In Part B question numbers 2 is compulsory. Answer any one full question from 3 and 4, 5 and 6, 7 and 8 & 9 and 10.

**PART-A**

- 1 1.1 Refer to Fig. 1.1 and find the voltages  $V_{12}$ ,  $V_{23}$  and  $V_{31}$ .

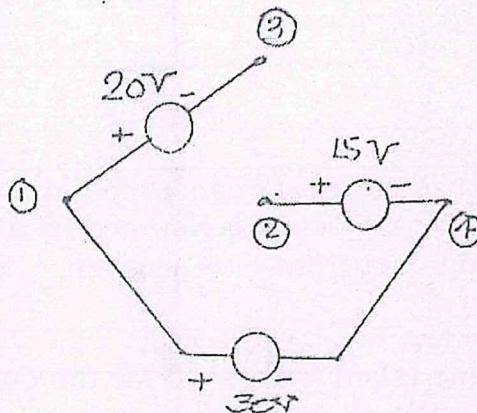


Fig. 1.1

- 1.2 An AC voltage of  $e = 200 \sin(314t - 30^\circ)$  Volts drives a current of  $i = 20 \sin(314t + 30^\circ)$  Amperes. What will be the power factor and the average power? 02
- 1.3 The necessary two conditions of a balanced three phase vectors are 02
- 1.4 What is hysteresis loss and how it is minimized in transformers? 02
- 1.5 A 3 - phase, 4 - pole, 400V, 50Hz induction motor runs at a speed of 1440rpm, calculate its slip. 02
- 1.6 The vectorial sum of three balanced currents is \_\_\_\_\_. 01
- 1.7 Mention the different types of single phase transformers. 01
- 1.8 Why the core loss is considered as constant loss in transformers? 01
- 1.9 What is the condition for maximum efficiency in a transformer? 01
- 1.10 What do you mean by slip? 01
- 1.11 The average value of a pure cosine wave having amplitude of 10V is \_\_\_\_\_ 01
- 1.12 The rms value of a sine wave is 10units, what is peak value? 01
- 1.13 Define voltage regulation of a transformer. 01
- 1.14 Why the efficiency of a transformer is always higher than other machines? 01
- 1.15 Why the induction motors are also called asynchronous motors? 01

**PART-B**

2 a	In the circuit shown in Fig. 2.a, find the potential difference across $x - y$ terminals and the power delivered by the $1\text{ Ohm}$ resistor.	08
b	State and explain Thevenin's theorem, using this theorem find the power dissipated to a load resistance of $10\text{ Ohms}$ in the circuit shown in Fig. 2.b	08
3 a	Show that the average power consumed in an AC circuit is $VI\cos\phi$ .	06
b	Show that the average power consumed by a pure inductor is zero.	04
c	An alternating current is given by : $i = 10 \sin 942t \text{ A}$ . Determine: i) frequency, ii) the time taken from $t = 0$ for the current to reach a value of $6\text{A}$ for the first and second time, iii) the energy dissipated when the current flows through a $20\text{ Ohm}$ resistor for $30\text{ minutes}$ .	06
	<b>OR</b>	
4 a	Draw and explain the vector diagram of an $R - L - C$ series circuit excited by a supply of $E$ volts when: i) $X_L = X_C$ , ii) $X_L > X_C$ , iii) $X_L < X_C$ .	08
b	Find the value of $R$ and $C$ in the circuit shown in Fig. 4.b, so that $V_b = 3V_a$ and $V_b$ are in quadrature. Also find the current $I$ .	08
	Fig. 4.b	08

5	a	Write the mathematical representation of three phase voltages with i) instantaneous values, ii) RMS values, iii) vector diagrams.	08																																								
	b	Show that two watt meters are sufficient to measure three phase power with a delta connected load. <b>OR</b>	08																																								
6	a	Show that the <i>e.m.f.</i> induced per turn is same for both primary and secondary windings of transformers.	08																																								
	b	The primary and secondary windings of a $500kVA$ transformer have resistances of $0.42$ and $0.0019\text{ Ohm}$ respectively. The primary and secondary voltages are $11000$ and $400V$ respectively and the core loss is $2.9kW$ . Assuming the power factor of $0.8$ calculate the efficiency at full load.	08																																								
7	a	Explain the principle of torque production in three phase induction motors.	05																																								
	b	Draw the typical torque slip characteristics of wound rotor induction motor and mark all the salient points on it.	05																																								
	c	A $6 - \text{pole}$ induction motor is supplied by a $3 - \text{phase}, 50\text{Hz}$ supply has a rotor frequency of $2.3\text{ Hz}$ . Calculate: i) the percentage slip, ii) speed of the rotor. What will be these values if the stator is wound for $4$ poles?	06																																								
		<b>OR</b>																																									
8	a	Explain why the starting torque is zero for a single phase induction motor, and how this will be produced.	05																																								
	b	Draw the electrical schematics of various types of single phase induction motors.	05																																								
	c	Draw and explain the rotor construction of the two types of three phase induction motors.	06																																								
9	a	Define the term 'Power System' and explain the same with the help of a block diagram showing all its components.	06																																								
	b	Differentiate between 'Fuse' and 'MCB' and mention the advantages and disadvantages.	06																																								
	c	What are preventive measures of electrical shock, explain.	04																																								
		<b>OR</b>																																									
10	a	What is earthing, why it is necessary and explain with diagram 'plate earthing'?	08																																								
	b	A domestic house uses the following appliances whose details are in the table below:																																									
		<table border="1"> <thead> <tr> <th>Sl. No.</th> <th>Appliances</th> <th>Power Rating</th> <th>Quantity Nos.</th> <th>Usage per day (Hrs)</th> </tr> </thead> <tbody> <tr> <td>1</td> <td>LED bulbs</td> <td><math>9\text{ W}</math></td> <td>10</td> <td>4</td> </tr> <tr> <td>2</td> <td>LED tube lights</td> <td><math>20\text{ W}</math></td> <td>3</td> <td>6</td> </tr> <tr> <td>3</td> <td>Geysers</td> <td><math>2\text{ kW}</math></td> <td>2</td> <td>1</td> </tr> <tr> <td>4</td> <td>Water pump</td> <td><math>500\text{ W}</math></td> <td>1</td> <td>2</td> </tr> <tr> <td>5</td> <td>Ceiling fans</td> <td><math>55\text{ W}</math></td> <td>6</td> <td>3</td> </tr> <tr> <td>6</td> <td>Mixer grinder</td> <td><math>1200\text{ W}</math></td> <td>1</td> <td>1</td> </tr> <tr> <td>7</td> <td>Induction top</td> <td><math>1500\text{ W}</math></td> <td>2</td> <td>6</td> </tr> </tbody> </table>	Sl. No.	Appliances	Power Rating	Quantity Nos.	Usage per day (Hrs)	1	LED bulbs	$9\text{ W}$	10	4	2	LED tube lights	$20\text{ W}$	3	6	3	Geysers	$2\text{ kW}$	2	1	4	Water pump	$500\text{ W}$	1	2	5	Ceiling fans	$55\text{ W}$	6	3	6	Mixer grinder	$1200\text{ W}$	1	1	7	Induction top	$1500\text{ W}$	2	6	
Sl. No.	Appliances	Power Rating	Quantity Nos.	Usage per day (Hrs)																																							
1	LED bulbs	$9\text{ W}$	10	4																																							
2	LED tube lights	$20\text{ W}$	3	6																																							
3	Geysers	$2\text{ kW}$	2	1																																							
4	Water pump	$500\text{ W}$	1	2																																							
5	Ceiling fans	$55\text{ W}$	6	3																																							
6	Mixer grinder	$1200\text{ W}$	1	1																																							
7	Induction top	$1500\text{ W}$	2	6																																							
			08																																								

Question No		Marks
1.1	$V_{12} = 15V, V_{23} = 5V, V_{34} = 10V$	
1.2	$\phi = 60^\circ \quad pf = \cos 60 = 0.5, P = \frac{200}{\sqrt{2}} \cdot \frac{20}{\sqrt{2}} \cos 60 = 1000W$	
1.3.	Equal magnitude and $120^\circ$ phase angle separation	
1.4	Due to the magnetic reversal in the core the molecular friction results in power loss in heating the core so minimum high permeability core is used.	
1.5	$\delta = \frac{\text{NS} - N}{\text{NS}} = \frac{1500 - 1400}{1500} \quad \text{NS} = \frac{120 \times 50}{4} = 1500 \mu\text{m}$ <u><math>= 0.06667\%</math></u>	
1.6	Vectorial sum is zero	2x5
1.7	Core type and shell type	
1.8	Core loss is constant as the Voltage V and frequency are fixed/constant	
1.9	Condition for max. efficiency is $I_{rot} / I_{rot} = C_{eul}$	
1.10	Slip is the ratio of Srf speed to Syn-speed	
1.11	The avg value of cosine wave $= \frac{2V_m}{\pi} = \frac{20}{\pi} V$	
1.12	$V_{peak} = \sqrt{2} V_{rms} = \sqrt{2} \times 10 = 14.14 \text{ units}$	
1.13	It is the change in the Sec. t.v. between NL and PL expressed as a percentage of PL t.v. at a given power factor	
1.14	$\eta$ is high, as there are no mechanical losses	
1.15	I m/s never runs at Syn-speed hence the name Asynchronous motor	1x10

Question No		Marks
2(a)	<p><math>I_1 = \frac{2}{5} = 0.4A</math></p> <p><math>I_2 = \frac{4}{8} = 0.5A</math></p> $V_{xy} - 3I_1 + 4 - 3I_2 = 0$ $V_{xy} = 3I_1 - 4 + 3I_2 = 3 \times 0.4 - 4 + 3 \times 0.5 =$ $\underline{V_{xy} = -3.7V}$	
(b)	<p><u>Thevenin's Theorem</u>: Any active, linear, bilateral network with two output terminals can be represented by a single voltage source in series with an equivalent single resistance (impedance) measured across these two terminals, where the single source is the Thevenin Source which is the OC Voltage across the terminals and the single impedance is the equivalent impedance measured across the same two terminals with all the internal sources set to zero.</p> <p><math>S_{ab}</math></p> <p><math>R_{th}</math>:</p> <p><math>V_{th}: I = \frac{100}{100} = 1A, V_{th} = 50I = 50V</math></p> <p><math>\therefore Th. Eq.: \frac{50}{75+10} I_L = \frac{50}{75+10} = 0.5882A</math></p> <p><math>P_L = I^2 R_L (0.5882)^2 \times 10 = 3.4675</math></p>	
3(a)	<p>The average power in an AC circuit is <math>VI \cos \phi</math>.</p> <p>If <math>v = V_m \sin \omega t</math>, <math>i = I_m \sin(\omega t + \phi)</math></p> <p><math>P = vi = V_m I_m \sin \omega t \cdot \sin(\omega t + \phi)</math>.</p> <p><math>P = \int p dt = VI \cos \phi</math></p>	

COURSE CODE:

COURSE:

Marks

Question No		Marks
3(b)	<p>The average Power Consumed by an inductor is zero  <math>V_2 V_m \sin \omega t, i = I_m \sin(\omega t - 90^\circ)</math> (as <math>I \ll V</math>)  <math>P = V_i i = V_m I_m \sin \omega t \sin(\omega t - 90^\circ)</math>  <math>= -V_m I_m \sin^2 \omega t</math> const</p> <p><u><math>P = \int V i dt = 0</math></u></p>	
(c)	<p><math>i = 10 \sin 942t</math>      <math>\omega = 942</math></p> <p>(i) <math>f = \frac{\omega}{2\pi} = \frac{942}{2\pi} = 150 \text{ Hz}</math></p> <p>(ii) <math>\theta = 10 \sin 942t</math></p> <p><math>\sin 942t_1 = 0.6 \text{ rad}</math></p> <p><math>t_1 = \frac{\sin^{-1} 0.6}{942} = 0.68 \text{ ms}</math></p> <p>for 2nd value <math>t_2 = t_1 + T = 0.68 + 6.67 = 7.35 \text{ ms}</math></p> <p>(iii) Energy = <math>I^2 R t</math> Wsec  <math>= \left( \frac{10}{\sqrt{3}} \right)^2 \times 20 \times \frac{30}{60} \text{ J} = 0.5 \text{ kwh}</math></p>	
4(a)	<p>Diagram of a series RLC circuit connected to an AC source.</p> <p>(i) <math>X_L &gt; X_C</math> <math>\phi &lt; 0^\circ</math></p> <p>Phasor diagram showing <math>V_R</math>, <math>V_L</math>, and <math>V_C</math> in series. <math>V = V_R + jV_L</math>. <math>\phi &lt; 0^\circ</math> indicates <math>V_L</math> leads <math>V_R</math>.</p> <p>(ii) <math>X_L &gt; X_C</math></p> <p>Phasor diagram showing <math>V_R</math>, <math>V_L</math>, and <math>V_C</math> in series. <math>V = V_R + jV_L</math>. <math>\phi \text{ lag.}</math> indicates <math>V_L</math> lags <math>V_R</math>.</p> <p>(iii) <math>X_L \approx X_C</math></p> <p>Phasor diagram showing <math>V_R</math>, <math>V_L</math>, and <math>V_C</math> in series. <math>V = V_R + jV_L</math>. <math>\phi \text{ lead.}</math> indicates <math>V_L</math> leads <math>V_R</math>.</p>	

one line explanation.

Question No		Marks
4(b)	<p>Diagram of a circuit with three parallel branches. The left branch contains a voltage source <math>240\text{V}, 50\text{Hz}</math> and an inductor <math>\text{L} = 6\text{H}</math>. The middle branch contains a resistor <math>R</math> and a capacitor <math>C</math> in series. The right branch contains a voltage source <math>-V_a</math>. The total current <math>I</math> is shown entering the left branch.</p> <p>Equations derived:</p> $X_L = 314 \times 0.025 = 8\Omega$ $V_b = 3V_a$ $V_b = 3V_C$ <p>Vector diagram showing <math>V_a</math> as the reference, <math>V_b</math> is at <math>90^\circ</math>, and <math>V</math> is at <math>180^\circ</math>.</p> $V = 3V_a - jV_C = V_a(3-j1) \Rightarrow 3.1623 V_a \angle -18.13^\circ$ $3.1623 V_a = 240 \therefore V_a = 75.89\text{V}, V_b = 227.67\text{V}$ $I = \frac{V_b}{Z_b} = \frac{227.67}{6+j8} = 22.77 \angle -53.13^\circ \text{ A.}$ $Z_a = \frac{V_a}{I} = \frac{75.89 \angle -90^\circ}{22.77 \angle -53.13} = 3.33 \angle 36.87^\circ \Omega$ $= (2.66-j2)\Omega$ $\therefore R = 2.66\Omega$ $X_C = 2\Omega = \frac{1}{314C} \therefore C = \frac{1}{314 \times 2} = 1592 \mu\text{F}$	
5(a)	<p>(i) <math>\bar{V}_{R2} = V_R \sin \omega t</math></p> $\bar{V}_y = V_y \sin(\omega t - 120^\circ)$ $\bar{V}_B = V_B \sin(\omega t + 120^\circ)$ <p>Diagram of a voltage source with magnitude <math>V_R</math> and phase angle <math>120^\circ</math> relative to the horizontal axis.</p> <p>(ii) <math>\bar{V}_{R2} = V_R \angle 0^\circ</math></p> $V_y = V_y \angle -120^\circ$ $V_B = V_B \angle 120^\circ$	
(b)	<p>Diagram of a three-phase system with resistors <math>R</math> and inductors <math>\text{L}</math> in each branch. The voltage across the first branch is <math>V_{R1}</math> and across the second branch is <math>V_{R2}</math>. Currents <math>I_R</math> and <math>I_B</math> are shown.</p> <p>Equations derived:</p> $\omega_1 = V_{R1}/(IR) \cos \angle \frac{IR}{V_{R1}}$ $\omega_2 = V_{B2}/(IB) \cos \angle \frac{IB}{V_{B2}}$ $I_R = I_{R1} - I_{B2}$ $I_B = I_{B2} - I_{R1}$	

COURSE CODE:

COURSE:

Marks

Question No		Marks
	<p> <math>W_1 = V_L I_L \cos(30^\circ + \phi)</math>  <math>W_2 = V_L I_L \cos(30^\circ - \phi)</math>  <math>\underline{W_1 + W_2 = \sqrt{3} V_L I_L \cos \phi}</math> </p> <p>(a) Enf Egn. <math>E_1 = 4.44 f\phi_m N_1</math> Volts. (P.B derive)  <math>\&amp; E_2 = 4.44 f\phi_m N_2</math> Volts  <math>\frac{E_1}{N_1} = 4.4 f\phi_m = \frac{E_2}{N_2}</math> Hence Enf per turn is same for both phases. See.</p> <p>(b) Soln kVA, <math>E_1 = 11000V, E_2 = 400</math>.  <math>I_{12} = \frac{500 \times 10^3}{11000} = 45.45A, I_{22} = \frac{500 \times 10^3}{400} = 1250A</math>  <math>P_{n. core} = I^2 R_{12} (45.45)^2 \times 0.42 = 867.59W</math>  <math>\text{See core} = I^2 R_{22} (1250)^2 \times 0.059 = 2968.75W</math>  <math>\text{Total core} = 867.59 + 2968.75 = 3836.34W</math>  <math>\text{Core loss} = 2.95W</math>  <math>\text{Output} = 500 \text{ kVA} \times 0.8 = 400 \text{ kW}</math>  <math>\text{Input} = \text{Output} + \text{Total loss} = 400 + 3.836.34 = 406.736 \text{ kW}</math>  <math>\eta = \frac{\text{Output}}{\text{Input}} = \frac{400}{406.736} \times 100 = \underline{98.34\%}</math> </p>	

Question No		Marks
F(b)	<p>Principle of torque production in 3 ph IM's.</p> <p>Whenever a balanced three emfs are applied to a balanced set of three windings there sets up a revolving magnetic field which revolves electrically at a speed called synchronous speed given by</p> $N_s = \frac{120f}{P}$ <p>where <math>f</math> is the freq of the applied emf and <math>P</math> the total no. of poles for which the stator windings are wound. In this revolving field if a closed coil system mounted on a freely rotating cylinder is placed, the revolving stator flux cuts the stationary coils, inducing an emf in these coils. As the coils are shorted (closed) there sets up a current which in turn establishes a second flux. These two fluxes interact resulting in a force acting on the rotor coil (tangential force) which makes the rotor to rotate in the direction of the stator field but cannot catch up the stator speed. The rotor speed is always less than the stator speed causing a slip.</p> <p>b)</p>	

COURSE CODE:



COURSE:

Question No		Marks
6(a)	<p><math>P=6, f = 50 \text{ Hz} \Rightarrow f_r = 2.3 \text{ Hz}</math></p> <p>(i) <math>S_{\text{cp}} = \frac{f_r}{f} = \frac{2.3}{50} = 0.046 \text{ or } 4.6\%</math>.</p> <p>(ii) <math>N_s = \frac{120f}{\phi} = \frac{120 \times 50}{\pi} = 1885 \text{ rpm}</math>.</p> <p><math>N = N_s(1-s) = 1885 (1-0.046) = 1800 \text{ rpm}</math>.</p> <p>If <math>P=4, N_s = 1500</math>.</p> <p><math>N = 1500(1-0.046) = 1431 \text{ rpm}</math>.</p>	
8(a)	<p>Whenever a coil is excited by 1φ AC Supply there will not be any revolving magnetic field as a result the torque is zero at the starting. Hence as it is 1φ IM are not starting. In order to create a rotating self starting. We introduce one more coil in parallel with the main winding, their planes are at 90°. The two fluxes in quadrature set up a field which revolves (Double field Reversal) thereby torque is produced in the starting.</p> <p>(b)</p> <p><u>Types of 1φ Ims.</u></p> <ul style="list-style-type: none"> <li>(1) Split phase/Resistance start.</li> <li>(2) Capacitor start.</li> </ul> <p>(1) Split phase/Resistance start.</p> <p>CS: Centrifugal Switch m - main wdg, sr - starting wdg.</p> <p>(2) Capacitor start.</p> <p>CS Rsr BjXsr C</p> <p>(3) Capacitor Start &amp; Capacitor run.</p> <p>Cr = Capacitor run Cs = Capacitor start,</p>	

COURSE CODE:

COURSE:

UG

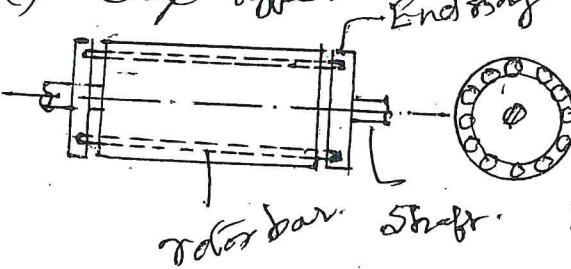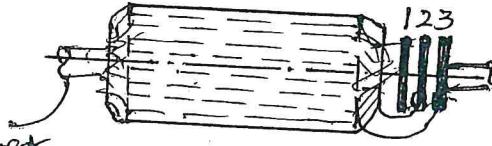Question No		Marks
8C	<p><u>Rotors of 3Ph IMs</u></p> <p>(i) Cage type.</p>  <p>(ii) Wound rotor</p> 	
Ques	<p><u>Power System</u>: It is the combination of Electrical Power generation, transmission and distribution.</p> <pre>     graph LR       A[Power Generation] --&gt; B[Power Transmission]       B --&gt; C[Distribution]       style A fill:#fff,stroke:#000,stroke-width:1px       style B fill:#fff,stroke:#000,stroke-width:1px       style C fill:#fff,stroke:#000,stroke-width:1px     </pre> <p>11 KV      220 KV      11 KV</p>	
	<p>Power is generated (Transformed) at generating stations (Hydro, Thermal &amp; Nuclear) at 11 KV and the voltage is stepped up to 220 KV or 400 KV through step-up transformer and transmitted over long distances and stepped down to 66 KV and then 11 KV for distribution. Three phase power generation &amp; transmission</p>	
Ques	<p><u>Fuse</u>: - A protective element (wire) which fuse out when the current through this exceeds its rating. It need to be replaced everytime.</p>	
	<p><u>MCB</u>: Miniature circuit breaker is an automatic device which trips off the circuit when the current through it exceeds its preset value. It can be reset after the fault is cleared</p>	

Question No		Marks
9(a)	<p>Preventive measures for electric shocks.</p> <ul style="list-style-type: none"> <li>(1) Insert plastic safety caps in all unused electrical outlets if small children are at home.</li> <li>(2) Do not plug too many things in a single outlet.</li> <li>(3) Periodic inspection of electrical wiring and sockets.</li> <li>(4) Replace old electrical points/gadgets.</li> <li>(5) Proper grounding is to be maintained.</li> <li>(6) Wear rubber shoes and gloves while operating on electrical equipment.</li> <li>(7) Do not touch electrical gadgets with wet hands.</li> </ul>	
10(a)	<p>Earthing is a process of creating a least resistance path for any fault current to occur due to the failure of insulation or any other reason.</p> <p>It is necessary to safe guard the life of a person, when he touches the faulty device, it prevents severe electric shock as the major fault current is diverted to the earthing point.</p> <p>With explanation.</p>	

Question No		Marks
(10b)	<p>LED bulbs</p> <ol style="list-style-type: none"> <li>1) <math>10 \times 9 \times 4 \times 10^3 = 0.36 \text{ kWhr}</math></li> <li>2) LED tube lights <math>3 \times 20 \times 6 \times 10^3 = 0.36 \text{ kWhr}</math></li> <li>3) Geysers : <math>2 \times 2 \times 5 = 1 \text{ kWhr}</math></li> <li>4) Water Pump : <math>0.5 \times 1 \times 2 = 1 \text{ kWhr}</math></li> <li>5) Fan : <math>55 \times 6 \times 3 \times 10^3 = 0.99 \text{ kWhr}</math></li> <li>6) Mixer : <math>1.2 \times 1 \times 1 = 1.2 \text{ kWhr}</math></li> <li>7) Induction Stove : <math>1.5 \times 2 \times 6 = 18 \text{ kWhr}</math></li> </ol> <p>Total Consumption/day = <math>25.91 \text{ kWhr}</math></p> <p>Monthly Consumption : <math>25.91 \times 30 = 777.3 \text{ Units}</math></p> <p>At the rate of Re 7/- per unit</p> <p>Total Amount = <math>777.3 \times 7 = 5441.10 \text{ Rs}</math></p> <p>8% Tax <math>\Rightarrow 435.30 \text{ Rs}</math></p> <p>Total Monthly Bill : <math>5441.10 + 435.30</math>  <math>\underline{\underline{= 5876.40 \text{ Rs}}}</math></p> <p>verified varadg/6. 06/03/2024.</p>	